

FREE

India's #1 Learning Platform

Start Complete Exam Preparation

Trusted by 1,86,00,449+ Students

Daily Live
MasterClassesPractice
Question BankMock Tests
& Quizzes

Download App



Question

[View this Question Online >](#)

Two resistors, one of $10\ \Omega$ and the other of $15\ \Omega$, are connected in parallel. This combination is connected in series with a $24\ \Omega$ resistor and a $12\ \text{V}$ battery. The current in the $15\ \Omega$ resistor is:

This question was previously asked in

RRB ALP Electronics Mechanic 21 Jan 2019 Official Paper (Shift 3)

Get PDF

Attempt Online

[View all RRB ALP Papers >](#)1. $0.40\ \text{A}$ 2. $0.24\ \text{A}$ 3. $0.12\ \text{A}$ 4. $0.16\ \text{A}$ **Answer** (Detailed Solution Below)Option 4 : $0.16\ \text{A}$

Crack State + Central Combo - Bengal Tiger with India's Super Teachers

FREE Demo Classes Available*

Explore Supercoaching For FREE



Detailed Solution

CONCEPT:

- **Resistance:** The measurement of the **opposition of the flow of electric current** through a **conductor** is called **resistance** of that conductor. It is denoted by **R**.

There are mainly **two ways** of the combination of resistances:


- **Resistances in series combination:** When two or more resistances are connected one after another such that the same current flows through them are called as resistances in series.



The **net resistance/equivalent resistance (R)** of resistances in series is given by:

Equivalent resistance, $R = R_1 + R_2$

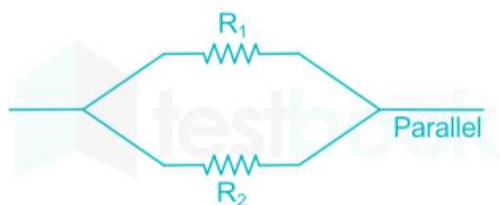- **Resistances in parallel combination:** When the terminals of two or more resistances are connected at the same two points and the potential difference across them is equal is called resistances in parallel.



The **net resistance/equivalent resistance(R)** of resistances in parallel is given by:

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

- **Ohm's law:** At constant temperature and other physical quantities, the **potential difference** across a current-carrying wire is directly proportional to the current flowing through it.

$$V = R I$$

Where V is the **potential difference**, R is **resistance** and I is **current**.


CALCULATION:

Given that:

$$R_1 = 10\ \Omega \text{ and } R_2 = 15\ \Omega$$

$$\text{Resistance in series (R')} = 24\ \Omega$$
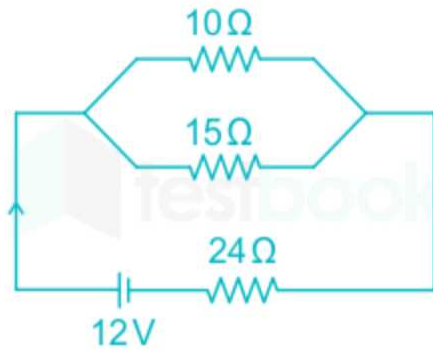
$$\text{Potential difference (V)} = 12\ \text{V}$$



The **net Resistance in Parallel combination** is given by:

$$1/R = 1/R_1 + 1/R_2$$

$$1/R = 1/10 + 1/15$$

$$\text{So } 1/R = 5/30$$

$$\text{Hence } R = 6\ \Omega$$

The combination is connected in series with a 24 Ω resistor, so the new net resistance of the circuit will be:

$$\text{New Total Resistance} = 6 + 24 = 30\ \Omega$$

Use Ohm's law:

$$\text{Electric current (I)} = V/R = 12/30 = 0.4\ \text{A}$$

$$\text{Now, Potential across } 24\ \Omega \text{ resistor} = 24 \times 0.4 = 9.6\ \text{V}$$

$$\text{Now, Potential across Parallel combination} = 12 - 9.6 = 2.4\ \text{V}$$

This is the electric Potential that will Reach both the Resistances of 15 Ω and 10 Ω.

By Using Ohm's law:

$$V = I \times R$$

$$2.4 = I \times 15$$

Electric current (I) = 0.16A. So option 4 is correct.